

Reg No.: \_\_\_\_\_

Name: \_\_\_\_\_

**APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY**

Fifth Semester B.Tech Degree Regular and Supplementary Examination December 2020

**Course Code:EE365****Course Name: DIGITAL SYSTEM DESIGN**

Max. Marks: 100

Duration: 3 Hours

**PART A***Answer all questions, each carries 5 marks.*

Marks

- |   |  |     |
|---|--|-----|
| 1 | What is Electronic design automation? What are its functions?                                    | (5) |
| 2 | Explain about Generics in VHDL with examples.  | (5) |
| 3 | What are the main components of an ASM chart? Explain.   | (5) |
| 4 | Write the VHDL code for a D Flip Flop with output Q and Qbar.                                    | (5) |
| 5 | What are the different constraints in RTL synthesis?   | (5) |
| 6 | Explain the concept of event driven simulation.  | (5) |
| 7 | Explain the necessity of testing digital systems.  | (5) |
| 8 | Discuss fault oriented test pattern generation and overall strategy for generating test pattern. | (5) |

**PART B***Answer any two full questions, each carries 10 marks.*

- |    |  |      |
|----|--|------|
| 9  | a) Explain the basic electrical properties of CMOS circuits.                             | (5)  |
|    | b) With the help of a neat block diagram explain how VHDL is used in the design process. | (5)  |
| 10 | a) Explain the implementation of NAND and NOR gate using CMOS Technology.                | (5)  |
|    | b) Write the VHDL code for a 2 to 4 Decoder.   | (5)  |
| 11 | Explain structural style of modelling in VHDL with suitable examples.                    | (10) |

**PART C***Answer any two full questions, each carries 10 marks.*

- |    |  |      |
|----|--|------|
| 12 | a) Design a state machine with two D Flip-Flops and one input X, when X=0 the state of the circuit remains the same, when X=1 the circuit goes through a transition from 00 to 01, then to 11, then to 10 and back to 00. Draw the logical diagram, state diagram, state stable and ASM chart. | (10) |
|----|--|------|

- 13 a) Write and explain the VHDL code for an n bit binary up counter. (5)  
b) Write the VHDL model for SIPO right shift register. (5)
- 14 a) Explain the steps involved in design of a (synchronous sequential) digital system. (5)  
b) Explain how a ROM chip is modelled using VHDL. (5)

**PART D**

*Answer any two full questions, each carries 10 marks.*

- 15 Explain simulation cycle of VHDL and its phases. (10)
- 16 Explain the main component of IEEE .1149.1 boundary scan test architecture. (10)
- 17 a) Explain built in self-test scheme. (5)  
b) Explain compilation and elaboration process in VHDL. (5)

\*\*\*\*