

02000CS203092001

Reg No.: \_\_\_\_\_

Name: \_\_\_\_\_

**APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY**

Third Semester B.Tech Degree (S,FE) Examination December 2020 (2015 Scheme)

**Course Code: CS203****Course Name: SWITCHING THEORY AND LOGIC DESIGN**

Max. Marks: 100

Duration: 3 Hours

**PART A***Answer all questions, each carries 3 marks.*

Marks

- 1 a)  $(162)_8 + (537)_8 =$  (3)  
 b)  $(37A)_{16} + (4B9)_{16} =$
- 2 Using truth table prove that  $(A+B)' = A'B'$  (3)
- 3 Perform subtraction using 2's complement method. (3)  
 a)  $(100)_2 - (110000)_2$   
 b)  $(11010)_2 - (1101)_2$
- 4 Express the given function in sum of minterms and product maxterms form. (3)  
 $F(A,B,C) = C(A'+B) + B'C$

**PART B***Answer any two full questions, each carries 9 marks.*

- 5 a) Perform the following conversions. (5)  
 i)  $(231B)_{16} = ( )_2$   
 ii)  $(574.32)_{10} = ( )_2$   
 iii)  $(10110011.01)_2 = ( )_8$   
 iv)  $(107)_8 = ( )_{10}$   
 v)  $(2671)_{10} = ( )_{16}$
- b) Convert the decimal number  $5.62 \times 10^3$  to IEEE 754 standard single precision floating point binary number. (4)
- 6 a) Simplify the Boolean function F using the don't care conditions d, in SOP and POS forms. (5)  
 $F(A,B,C,D) = A'B'D' + A'CD + A'BC$   
 $d(A,B,C,D) = A'BC'D + ACD + AB'D'$
- b) The sum of all minterms of a Boolean function of  $n$  variables is 1. (4)  
 Prove the above statement for  $n=3$ .

- 7 a) Simplify the given function using Tabulation method and determine the prime implicants, essential prime implicants and the minimized Boolean expression. (9)

$$F(A,B,C,D) = \Sigma(0,2,6,8,9,10,11,13,15)$$

**PART C**

*Answer all questions, each carries 3 marks.*

- 8 Implement Exclusive-OR using only NAND gates. (3)
- 9 Draw the truth table and the logic circuit of a full adder. (3)
- 10 Explain race around condition in JK flip-flop. (3)
- 11 Draw the logic diagram of a D flip-flop using only NAND gates. Draw the characteristic table and obtain the characteristic equation. (3)

**PART D**

*Answer any two full questions, each carries 9 marks.*

- 12 a) A combinational circuit is defined by the following two functions. (5)
- $$F_1 = x'y' + xyz'$$
- $$F_2 = x' + y$$
- Design the circuit with a decoder and external gates.
- b) Implement the function  $F(A,B,C) = \Sigma(0,2,3,5)$  using a 2X1 MUX. (4)
- 13 a) Design a magnitude comparator that compares two 3 bit numbers A and B. (5)
- b) Design a circuit that implements an SR flip-flop using a D flip-flop. (4)
- 14 a) A sequential circuit has two flip-flops A and B and one input x. The flip-flop input functions are as follows. (9)
- $$J_A = xB, \quad K_A = xB'$$
- $$J_B = x'A', \quad K_B = x + A$$
- Obtain the state table, state diagram and state equations.

**PART E**

*Answer any four full questions, each carries 10 marks.*

- 15 a) Draw the circuit diagram of a 4-bit bidirectional shift register with parallel load and explain its working. (10)
- 16 a) Design a serial adder using a sequential-logic procedure (7)
- b) Explain the different types of ROMs. (3)
- 17 a) Design a counter with the following binary sequence: 0, 1, 3, 7, 6, 4 and repeat. (6)
- Use T flip-flops.
- b) Write an HDL code for a half adder in structural style of modelling. (4)

- 18 a) Explain PLA with a block diagram. (4)
- b) A combinational circuit is defined by the functions: (6)
- $$F_1(A,B,C) = \Sigma(3,5,6,7)$$
- $$F_2(A,B,C) = \Sigma(0,2,4,7)$$
- Implement the circuit with a PLA having three inputs, four product terms and two outputs.
- 19 a) Draw a flow chart and explain the addition and subtraction of two binary numbers in signed magnitude representation. (10)
- 20 a) Differentiate between synchronous and asynchronous counters. (4)
- b) Draw the circuit diagram of a 4- bit binary ripple counter and explain its working. (6)

\*\*\*\*