

Course Code: EC207**Course Name: LOGIC CIRCUIT DESIGN (EC, AE)**


Max. Marks: 100

Duration: 3 Hours

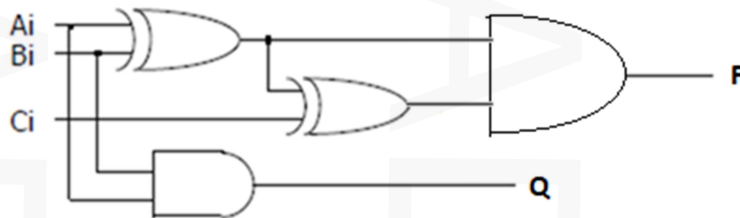PART A*Answer any two full questions, each carries 15 marks.*

Marks

- 1 a) Convert the decimal number 963 to its equivalent Octal, Hexadecimal, BCD, Gray, XS-3 codes. (10)
- b) Determine the Hamming code for the information 1101, with even parity. (5)
- 2 a) Simplify using K-map $F(a,b,c,d) = \sum m (3,7,11,13,15) + \sum d (0,12,14)$ and implement the circuit using NAND gates. (10)
- b) Write expression for P and Q. (5)



- 3 a) Develop a full-subtractor circuit using a 3-to-8 decoder and gates. (9)
- b) Consider two signed binary numbers $A=0111$ and $B=1000$ (B is in 2's complement form). Find $A+B$ and $A-B$. Use 2's complement method for subtraction. Justify your answer. (6)

PART B*Answer any two full questions, each carries 15 marks.*

- 4 a) Construct a 2 input NAND gate using CMOS. Explain its working with the help of truth table. (7)
- b) Explain Fan-in, Fan-out, Propagation delay, and Noise margin of logic families. (8)
- 5 a) Design a mod-5 synchronous up counter using JK FF. (10)
- b) Convert a D FF to T FF. (5)
- 6 a) Design a 3-bit ripple up counter using T FF and explain its working showing its timing diagram. (9)
- b) Build a full adder circuit using PLA. (6)

PART C

Answer any two full questions, each carries 20 marks.

- 7 a) Construct a 4 bit serial-in serial-out **left shift** register using JK FF. Describe its operation on every clock pulse. (8)
- b) Show the state table and Mealy model state diagram of JK FF. Derive its characteristic equation (12)
- 8 a) Design a 3-bit asynchronous up/down counter using JK FF that counts up when the mode $M=1$ and counts down when Mode=0. How does the circuit work (10)
- b) Explain the working of a twisted ring counter, with the help of timing diagrams. (10)
- 9 a) Design a circuit to detect the sequence 1010 with overlapping, using D FF. Draw the state diagram, state table, excitation table and the circuit (10)
- b) Minimize the state table using implication chart. (10)

| Present state | Next state | | Output | |
|---------------|------------|-----|--------|-----|
| | x=0 | x=1 | x=0 | x=1 |
| a | d | b | 0 | 0 |
| b | e | a | 0 | 1 |
| c | g | f | 0 | 1 |
| d | a | d | 1 | 0 |
| e | a | d | 1 | 0 |
| f | c | b | 0 | 0 |
| g | a | e | 1 | 0 |
