

Reg No.: _____

Name: _____

APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY
EIGHTH SEMESTER B.TECH DEGREE EXAMINATION(S), OCTOBER 2019

Course Code: EE464

Course Name: Flexible AC Transmission Systems

Max. Marks: 100

Duration: 3 Hours

PART A

Answer all questions, each carries 5 marks.

Marks

- | | | |
|---|---|-----|
| 1 | Name different FACTS devices with their circuit representations. | (5) |
| 2 | Why midpoint of a symmetrical transmission line is considered ideal for shunt compensation? | (5) |
| 3 | Differentiate between the working of TSR and TCR | (5) |
| 4 | Draw the phasor diagram of the 3 phase PAR | (5) |
| 5 | What is the basic principle of operation of STATCOM? | (5) |
| 6 | Draw the V-I characteristics of STATCOM and SVC and compare. | (5) |
| 7 | Draw the circuit configuration of SSSC | (5) |
| 8 | How to implement a UPFC using two voltage source converters? | (5) |

PART B

Answer any two full questions, each carries 10 marks.

- | | | |
|----|--|------|
| 9 | How power flow in an interconnected AC system can be controlled? What are the constraints in maximum line loading? | (10) |
| 10 | Compare between Static converter based and Passive Impedance based var generators | (10) |
| 11 | By shunt compensation the transient stability limit and power transfer capability can be is increased. How? | (10) |

PART C

Answer any two full questions, each carries 10 marks.

- | | | |
|----|--|-----|
| 12 | a) How a TSC can be implemented? Draw the schematic. | (5) |
| | b) What is the role of series inductor in a TSC? | (5) |
| 13 | a) What are the objectives of a voltage regulator and a phase angle regulator? | (4) |
| | b) How the concept of voltage regulator and phase angle regulator can be implemented? Explain with schematic and phasor diagram. | (6) |
| 14 | a) How a TCSC can be implemented? Draw its operating region. | (5) |

- b) How the continuous control of thyristor tap changing can be achieved? Draw the control scheme. (5)

PART D

Answer any two full questions, each carries 10 marks.

- 15 How SSSC can be controlled by direct control method? Explain with neat Schematic. (10)
- 16 Using the phasor diagrams explain the versatile transmission control capability of UPFC. (10)
- 17 What is interline power flow controller? With a schematic diagram, explain its working. (10)
