

Reg No.: _____

Name: _____

APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY

Seventh semester B.Tech examinations (S), September 2020

Course Code: EC461**Course Name: MICROWAVE DEVICES AND CIRCUITS**

Max. Marks: 100

Duration: 3 Hours

PART A*Answer any two full questions, each carries 15 marks.*

Marks

- | | | |
|---|---|------|
| 1 | a) What are TRAPATT diodes? Explain elaborately their principle of operation with neat diagram. | (10) |
| | b) What are the limitations of conventional solid state devices at microwaves | (5) |
| 2 | a) Discuss in detail the physical structure of MESFET and explain its principle of operation. | (10) |
| | b) Write a short note on one port negative resistance oscillator | (5) |
| 3 | a) Explain in detail Various modes of operation of Gunn Oscillators | (8) |
| | b) Derive the expression for available power gain of microwave amplifier | (7) |

PART B*Answer any two full questions, each carries 15 marks.*

- | | | |
|---|---|------|
| 4 | a) Explain in detail the concept of matching with lumped elements. | (10) |
| | b) Write a short note on S matrix | (5) |
| 5 | a) Explain the steps in designing a composite filter. Also write down the equations and draw the circuit for designing a composite low pass filter. | (10) |
| | b) Discuss the significance of $k-\beta$ diagram in filter characteristics | (5) |
| 6 | a) Explain the principle of single stub tuning | (7) |
| | b) Design a low pass constant K filter using image parameter method. | (8) |

PART C*Answer any two full questions, each carries 20 marks.*

- | | | |
|---|---|------|
| 7 | a) Explain the fabrication technique involved in Monolithic Microwave Integrated circuits. | (10) |
| | b) Discuss briefly about slot line. | (6) |
| | c) List down the advantages of planar transmission line. | (4) |
| 8 | a) Classify switches based on characteristics. Explain the basic configuration of PIN diode switches. | (12) |

- b) Explain the configuration of distributed ferrite circulators. (4)
- c) Write a short note on inductors. (4)
- 9 a) Differentiate strip line and microstrip line. (6)
- b) Explain attenuators with neat diagram. (10)
- c) Write a short note on hybrid MIC. (4)

ADR-ADR-ADR