

APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY

Fifth semester B.Tech degree examinations (S) September 2020

Course Code: EC361**Course Name: DIGITAL SYSTEM DESIGN**


Max. Marks: 100

Duration: 3 Hours

 PART A*Answer any two full questions, each carries 15 marks.*

Marks

- 1 a) Examine the clocked synchronous sequential network given below and obtain the excitation equation, excitation table, state transition table, state table and state diagram. (10)




- b) Draw the ASM chart for mod-8 down counters. (5)
- 2 a) Obtain a primitive flow table and minimal-row flow table for a fundamental mode asynchronous sequential network with two inputs x_1 , x_2 and one output z . (10)
The inputs x_1 and x_2 never change simultaneously. The output is same as x_2 if $x_1 = 1$. However if $x_1 = 0$, the output should remain fixed at its last value.
- b) With a transition table, explain the concept of critical race, non-critical race and cycle. (5)
- 3 a) Explain the three steps in state table reduction. (6)
- b) Find the reduced flow table for the following: (9)

PS	NS				Output (z)			
	Input State (x1x2)				Input State (x1x2)			
	00	01	10	11	00	01	10	11
A	Ⓐ	B	E	-	1	-	-	-
B	A	Ⓑ	-	H	-	0	-	-
C	G	-	Ⓒ	-	-	-	1	-
D	Ⓓ	F	C	-	0	-	-	-
E	A	-	Ⓔ	-	-	-	1	-
F	D	Ⓕ	-	H	-	0	-	-
G	Ⓖ	B	C	-	1	-	-	-
H	-	F	C	Ⓗ	-	-	-	1

 PART B

Answer any two full questions, each carries 15 marks.

- 4 a) What is an essential hazard? Explain its impact with the help of a logic diagram. (5)
 b) Examine the problem of switch bouncing and explain the remedial solution. (5)
 c) Explain the functionality of mixed operating mode circuit. (5)
- 5 a) Using Kohavi algorithm, find the test set to detect SA0 and SA1 faults in a circuit whose function is $f(a,b,c,d) = ad' + c'd + a'c$ (9)
 b) Find the test vectors for the SA0 and SA1 faults on each of the input lines by path sensitization method for the 3 bit parity checking logic circuit shown below: (6)



- 6 a) Describe Kohavi Algorithm for multiple fault detection (10)
 b) Explain clock skew? Differentiate between positive clock skew and negative clock skew. (5)

PART C

Answer any two full questions, each carries 20 marks.

- 7 a) In the context of PLA, explain the terms: i) growth faults ii) shrinkage faults iii) appearance faults iv) disappearance faults. (8)
 b) Use IISc algorithm to determine the essential prime cubes of the four-variable single-output function, $f = 2201 + 0102 + 0111 + 0110 + 2100$ (12)

- 8 a) With a diagram, describe the I/O block of XC4000 FPGA (8)
- b) Explain the following terms: i) PLA minimisation ii) PLA folding iii) Foldable Compatibility Matrix (9)
- c) Illustrate the XC4000 general interconnect structure. (3)
- 9 a) List the differences between FPGA and CPLD (2)
- b) With illustrations, describe the architecture of XC9500 CPLD family. (8)
- c) With suitable sketches, describe the internal structure of XC4000 CLB. (10)
