

**APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY**  
Third Semester B.Tech Degree (S,FE) Examination December 2020

**Course Code: EC201**

**Course Name: NETWORK THEORY**

Max. Marks: 100


Duration: 3 Hours

**PART A**


*Answer any two full questions, each carries 15 marks.*

Marks

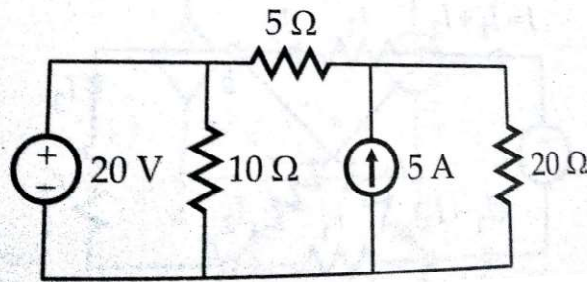
- 1 a) State and explain Thevenin's theorem and Norton's theorem. (4)
- b) Find the power loss across  $5\Omega$  for the given network by using mesh analysis. (5)



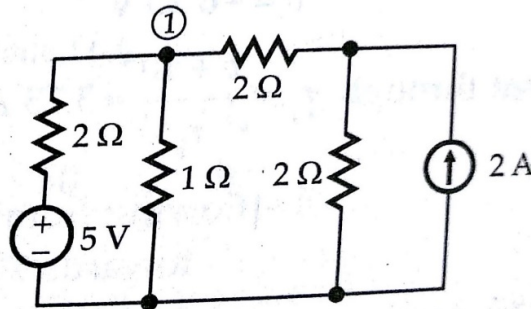- c) Find the current in  $1\Omega$  by nodal analysis. (6)



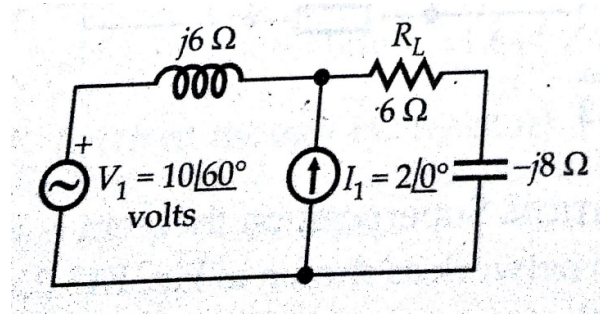- 2 a) Using super position theorem, find the current through  $6\Omega$  for the given network. (8)




- b) Explain Complete incidence matrix and fundamental cutset matrix with an example. (7)
- 3 a) State and prove Initial value theorem. (3)
- b) Find inverse Laplace transform of  $F(s) = \frac{50}{(s+1)(s+5)}$  (4)
- (c) Find the Laplace Transform of the following (8)
- (i)  $\cos(\omega t + \Theta)$  and (ii)  $(1 + 2t e^{-6t})^3$
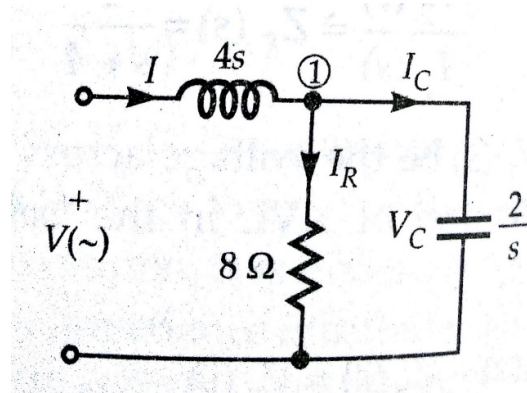
### PART B

*Answer any two full questions, each carries 15 marks.*

- 4 a) Solve the differential equation using Laplace Transform  $Y'' + 2Y' + 3Y = 0$  (8)  
Given  $y(0) = 1$  and  $y'(0) = 0$
- b) Given  $I(s) = \frac{3s}{(s+1)(s+3)}$  (7)  
Plot Pole zero plot and hence obtain  $i(t)$  from pole zero plot.
- 5 a) Write any five properties of driving point admittance functions. (5)
- b) A series RLC circuit with  $R = 300\Omega$ ,  $L = 1$  H and  $C = 100$  Micro Farad has a constant voltage of 50 V applied at  $t=0$ . Find maximum value of current. Assume zero initial condition. (6)
- c) A series RL circuit with  $R = 200\Omega$  and  $L = 20$  H is connected to a 250 V dc source. Find the transient current. (4)
- 6 a) Derive transient current and voltage responses of RL and RC Circuits energised by a dc voltage source of V volts. (10)
- b) Find Voltage Transfer function for the given network. (5)



### PART C

*Answer any two full questions, each carries 20 marks.*

- 7 a) Find the ABCD parameters for the given network. Given  $Z_{11} = 4 \Omega$ ,  $Z_{12} = 1 \Omega$ ,  $Z_{21} = 3 \Omega$  and  $Z_{22} = 3 \Omega$  (8)
- b) Explain hybrid parameters of two port network. (7)
- c) Explain dot convention in coupled coils. (5)
- 8 a) Explain series and parallel connections of two port networks. (8)
- b) Determine the interrelationship between hybrid and Z parameters. (6)
- c) Explain the following terms (6)
- (i) Bandwidth (ii) Q- factor and (iii) Selectivity
- 9 a) Two similar coupled coils of resistance  $5 \Omega$  and self inductance 1 H are in series. This is in series with a 100 Micro Farad Capacitor. A 220V, 50 Hz source energise the circuit. Draw the dotted equivalent circuit. Calculate the coefficient of coupling so that circuit behaves as a pure resistor. (8)
- b) Derive the output voltage expression for a single tuned circuit. (7)
- c) A double tuned circuit is tuned to a frequency of 750 Hz. when excited with voltage source at critical coefficient of coupling, the maximum voltage across  $C_2 = 20 \text{ V}$ . Find the coefficient of coupling and the source voltage. (5)
- Given  $Q_1 = 6$ ,  $Q_2 = 10$   $R_1 = 10 \Omega$  and  $R_2 = 90 \Omega$

\*\*\*\*