

Reg No.: _____

Name: _____

APJ ABDUL KALAM TECHNOLOGICAL UNIVERSITY
Third Semester B.Tech Degree Examination December 2020 (2019 Scheme)

Course Code: CST203

Course Name: LOGIC SYSTEM DESIGN

Max. Marks: 100

Duration: 3 Hours

PART A

Answer all questions. Each question carries 3 marks

		Marks
1	Convert $(456.78)_{10}$ to a) binary b) octal and c) hexadecimal	(3)
2	Write a) 1's complement and 2) 2's complement representations of (-126)	(3)
3	State and prove De Morgan's Theorem	(3)
4	Design a circuit using NAND gates for implementing EXCLUSIVE-OR function	(3)
5	Design a half adder circuit using any universal gate.	(3)
6	Draw the logic diagram of a 2×1 multiplexer circuit	(3)
7	Derive the characteristic equation of a D flip flop from its excitation table.	(3)
8	How is a sequential circuit different from a combinational circuit? Give an example for each circuit.	(3)
9	Distinguish between a ring counter and Johnson counter	(3)
10	When do you implement a combinational circuit using ROM and when do you implement a combinational circuit using PLA in preference to ROM.	(3)

PART B

Answer any one full question from each module. Each question carries 14 marks

Module 1

11	a) Convert i) $(13AF)_{16}$ to octal ii) $(10110101.101)_2$ to decimal	(6)
	b) Add i) BCD numbers 1567 and 968 ii) octal numbers 2376 and 5677	(8)
12	a) Perform the following operations using 2's complement representation	(10)
	i) $(-34) + (+21)$ ii) $(+26) - (-12)$ iii) $(-33) + (-22)$ iv) $(+45) - (+32)$	
	b) Convert i) (10011010) in 2's complement form to decimal	(4)
	ii) (10111001) in 1's complement form to decimal	

Module 2

13	a) Using K Map simplify the function	(8)
	$F(w, x, y, z) = \sum (0, 1, 2, 3, 5, 7, 8, 9, 10, 13, 15)$	
	b) Express the above function in product of maxterms form.	(6)

- 14 a) Using tabulation method simplify the function (8)
$$F(w,x,y,z) = \sum (0,2,4,5,6,7,8,12,13,14,15)$$

b) Express the following functions in a canonical form (6)
i) $F = D + BC'$ ii) $F = AB' + BC'$

Module 3

- 15 a) Design a full subtractor circuit. (6)
b) Design a code converter for converting a BCD to excess-3 code. (8)
- 16 a) Explain BCD adder using a block diagram. (7)
b) Design a 2 bit magnitude comparator. (7)

Module 4

- 17 a) With a logic diagram explain how a master slave flip flop overcomes race (7)
around problem.
b) Design a 2 bit synchronous counter. (7)
- 18 a) Draw the state diagram and logic diagram of a BCD ripple counter. (6)
b) Design a 3 bit synchronous up-down counter. (8)

Module 5

- 19 a) Explain the working of a 3 stage Johnson ring counter with a block diagram (7)
b) Explain the working of a 3 bit bidirectional shift register with parallel load. (7)
- 20 a) Illustrate the algorithm for addition and subtraction of two floating point (7)
numbers.
b) Illustrate the algorithm for addition and subtraction two binary numbers in (7)
sign magnitude form.
